

Design Example Using the NR263S

$V_{OUT} = 5\text{ V}$, $I_{OUT(MAX)} = 1\text{ A}$

DC/DC Converter

Contents

1. Introduction	3
2. Power Supply Features	3
3. Application	3
4. Design Example: Appearance	3
5. Design Example	4
5.1 Power Supply Specifications	4
5.2 Circuit Diagram	5
5.3 Bill of Materials	5
5.4 Pattern Layout Example	6
6. Performance Data	7
6.1 Start/Stop Operation	7
6.2 Overcurrent Protection	7
6.3 Circuit Current at No Load	8
6.4 Efficiency	9
6.5 Load Regulation	9
7. Operation Check	10
7.1 Startup Operation	10
7.2 Switching Operation	11
7.3 Output Ripple Voltage	12
7.4 Load Transient Reponse	12
Important Notes	13

1. Introduction

This document describes the design example of a power supply using the NR263S intended for the DC/DC converter that supports a 5 V/1 A (max.) output. The NR263S is a buck converter IC with a built-in power MOSFET. By using the peak current control method, the IC stably operates with a low ESR capacitor such as a ceramic capacitor.

The IC has the protections including overcurrent protection (OCP), undervoltage lockout (UVLO), and thermal shutdown (TSD).

This document contains the following: the specifications of the design example, circuit diagrams, the bill of materials, the setting examples of component constants, a pattern layout example, and the evaluation results of the power supply characteristics. For more details on the parts listed in this document, refer to the corresponding data sheets.


2. Power Supply Features

- Efficiency: 93% ($V_{IN} = 9\text{ V}$, $V_O = 5\text{ V}$, $I_O = 0.5\text{ A}$)
- Operation Modes:
 - Normal Operation: Current Mode PWM Control
 - Light Load Operation: Pulse Skipping Operation
- Few Components and Small Mounting Area
 - Built-in power MOSFET
 - Ceramic Capacitor can be used for Output Capacitor
 - Built-in Phase Compensation Circuit
- Soft Start Function
 - Soft-start Period Adjustment by External Capacitor
- Enable Function
- Protections
 - Overcurrent Protections (OCP): Drooping Type, Auto-restart
 - Thermal Shutdown (TSD): Auto-restart
 - Undervoltage Lockedout (UVLO)
 - Output Short Circuit Protection: Burst Oscillation Operation (Hiccup)

3. Application

- Audio Visual Equipment
- White Goods
- Auxiliary Power Supply
- Other Switched Mode Power Supplies (SMPS)

4. Design Example: Appearance

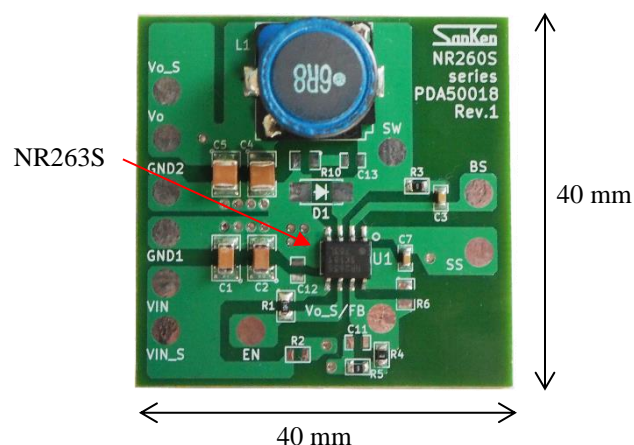

5. Design Example

5.1 Power Supply Specifications

Parameter	Symbol	Conditions	Min.	Typ.	Max.	Unit
Input						
Input Voltage	V_{IN}		8	—	31	V
Output						
Rated Voltage	V_{OUT}		—	5	—	V
Rated Current ⁽¹⁾	I_{OUT}		—	—	1	A
Output Ripple Voltage	V_{RIPPLE}	$V_{OUT} = 5\text{ V}$, $I_{OUT} = 1\text{ A}$, $C4 = 22\ \mu\text{F}$, $C5 = 22\ \mu\text{F}$ ⁽²⁾	—	20	—	mV _{P-P}
Efficiency	η	$V_{IN} = 9\text{ V}$, $I_{OUT} = 0.5\text{ A}$, $T_A = 25\text{ }^\circ\text{C}$	—	93	—	%
Environment						
Conduction Noise	—	$T_A = 25\text{ }^\circ\text{C}$	As per CISPR22B / EN55022B			—
Temperature						
Operating Ambient Temperature ⁽¹⁾	T_{OP}		-40	—	85	$^\circ\text{C}$

⁽¹⁾ Must be used in the range of thermal derating. For details, refer to the NR263S data sheet.

⁽²⁾ Low ESR ceramic capacitors can be used for C4 and C5.

5.2 Circuit Diagram

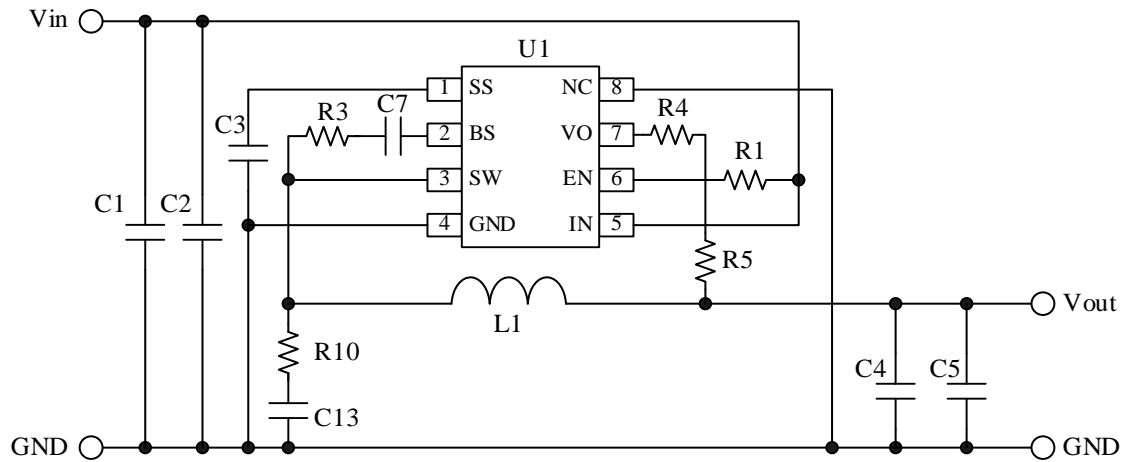


Figure 5-1. Circuit Diagram


5.3 Bill of Materials

Part Symbol	Part Type	Ratings	Remarks
C1	Chip ceramic capacitor	10 μ F, 50 V, 3216	
C2	Chip ceramic capacitor	10 μ F, 50 V, 3216	
C3	Chip ceramic capacitor	0.1 μ F, 50 V, 1608	
C4	Chip ceramic capacitor	22 μ F, 25 V, 3225	Low ESR type
C5	Chip ceramic capacitor	22 μ F, 25 V, 3225	Low ESR type
C7	Chip ceramic capacitor	0.047 μ F, 50 V, 1608	
C13	Chip ceramic capacitor	Open	Adjustment capacitor
L1	Inductor	6.8 μ H	SLF12575T-6R8N5R9-PF (TDK)
R1	Chip resistor	100 k Ω , 0.1 W, 1608	
R3	Chip resistor	0 Ω , 1608	Adjustment capacitor
R4	Chip resistor	0 Ω , 1608	Jumper
R5	Chip resistor	0 Ω , 1608	Jumper
R10	Chip resistor	Open	Adjustment capacitor
U1	Buck Converter IC	SOP8	NR263S (Sanken)

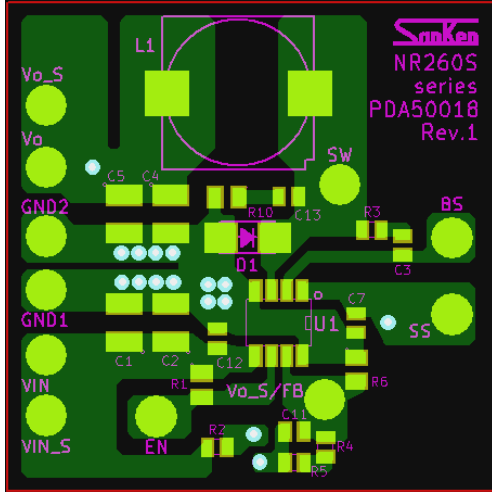
5.4 Pattern Layout Example

PCB dimensions: 40 mm × 40 mm.

Note that the pattern layout example only uses the parts illustrated in the circuit diagram below because this board is used for some other products.



(a) Top View

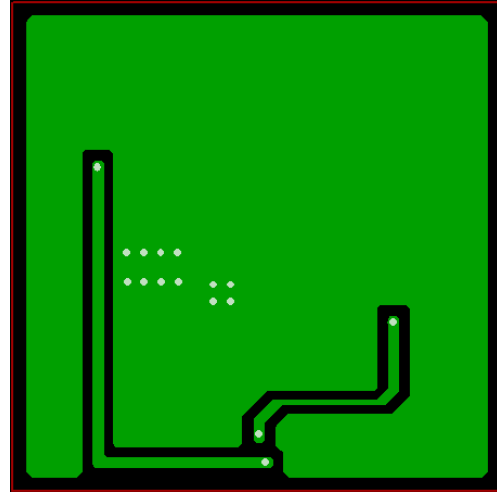

(b) Bottom View

Figure 5-2 Pattern Layout Example

6. Performance Data

All the performance data contained in this document were measured at a room temperature. Unless specifically noted, $V_{IN} = 12\text{ V}$, $V_{OUT} = 5\text{ V}$.

6.1 Start/Stop Operation

The NR263S has the undervoltage lockout. Figure 6-1 shows the startup characteristics of output voltage vs. input voltage (i.e., the IN pin voltage). When $V_{OUT} = 5\text{ V}$, the input voltage must be set to $\geq 8\text{ V}$.

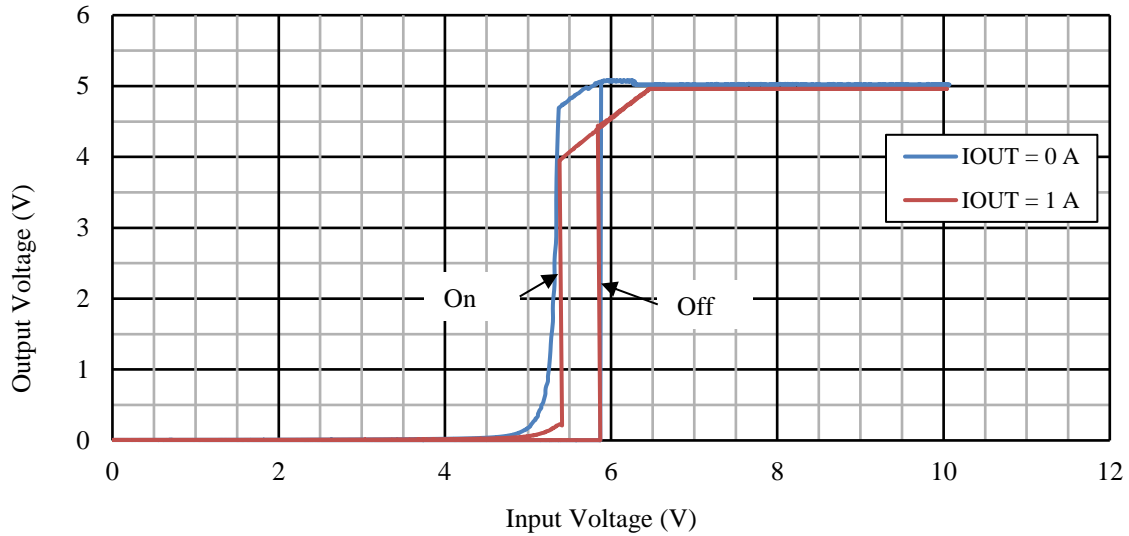


Figure 6-1. Output Voltage vs. Input Voltage

6.2 Overcurrent Protection

The NR263S has the drooping overcurrent characteristic. Figure 6-2 shows the overcurrent characteristics according to the input voltage.

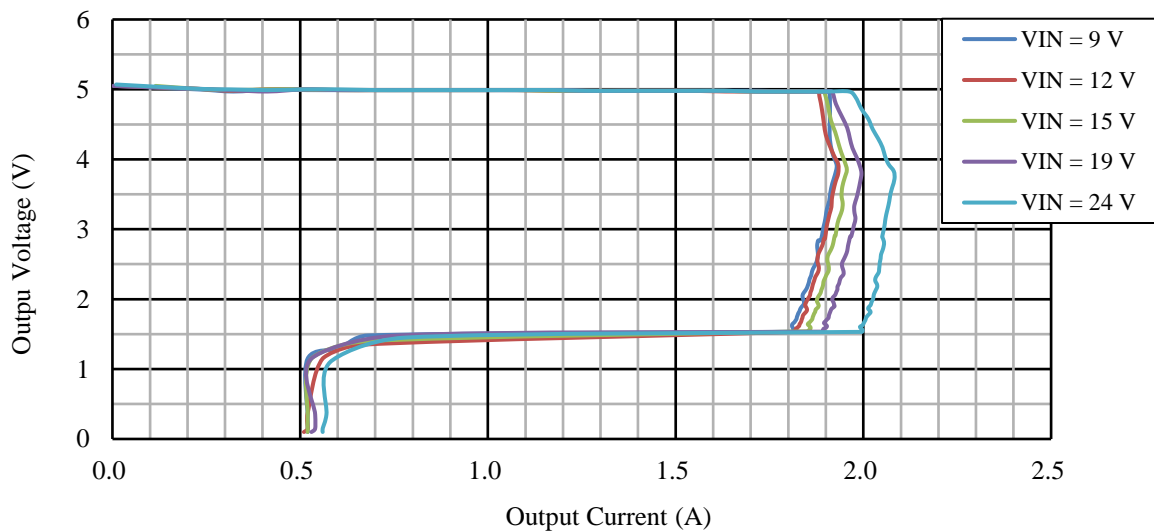


Figure 6-2. Overcurrent Protection Characteristics

6.3 Circuit Current at No Load

Figure 6-3 and Figure 6-4 show the IN pin input voltage dependence at no load ($V_{OUT} = 5\text{ V}$, $I_{OUT} = 0\text{ A}$) in operation and non-operation, respectively.

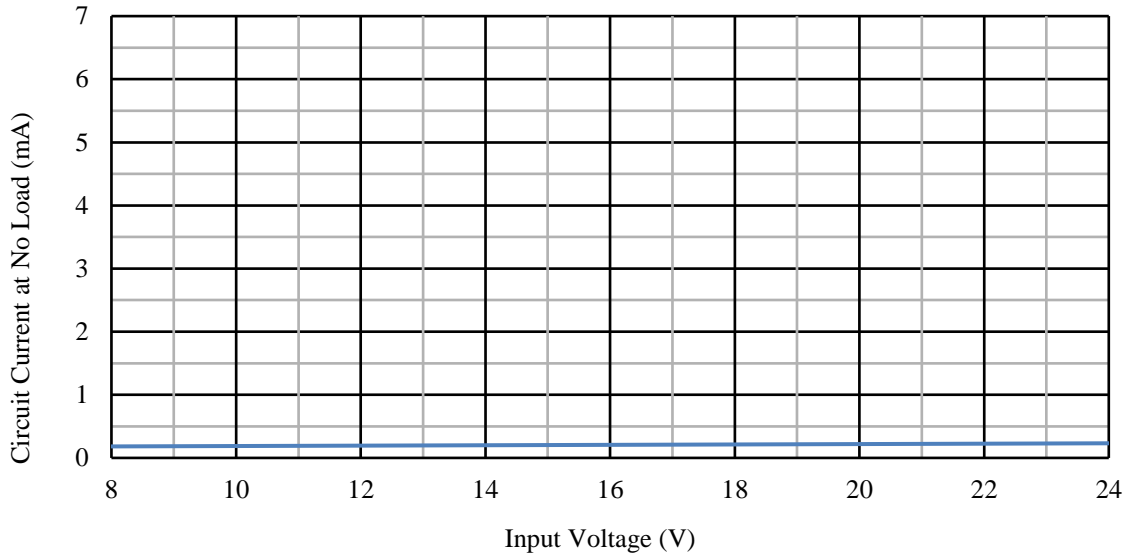


Figure 6-3. Circuit Current at No Load vs. Input Voltage in Operation

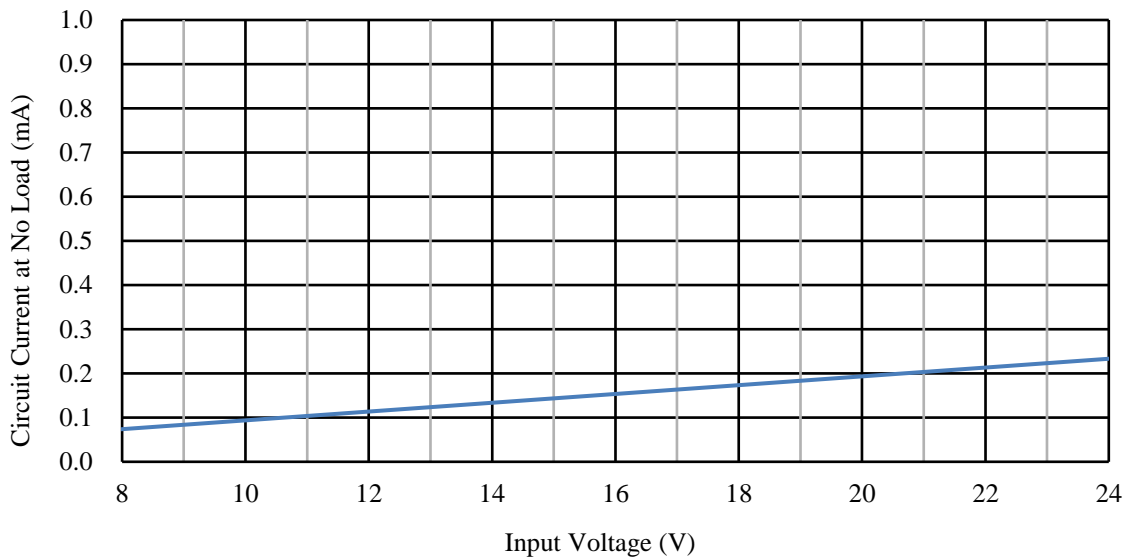


Figure 6-4. Circuit Current at No Load vs. Input Voltage in Non-operation

6.4 Efficiency

Figure 6-5 shows the characteristics of power supply efficiency vs. output current.

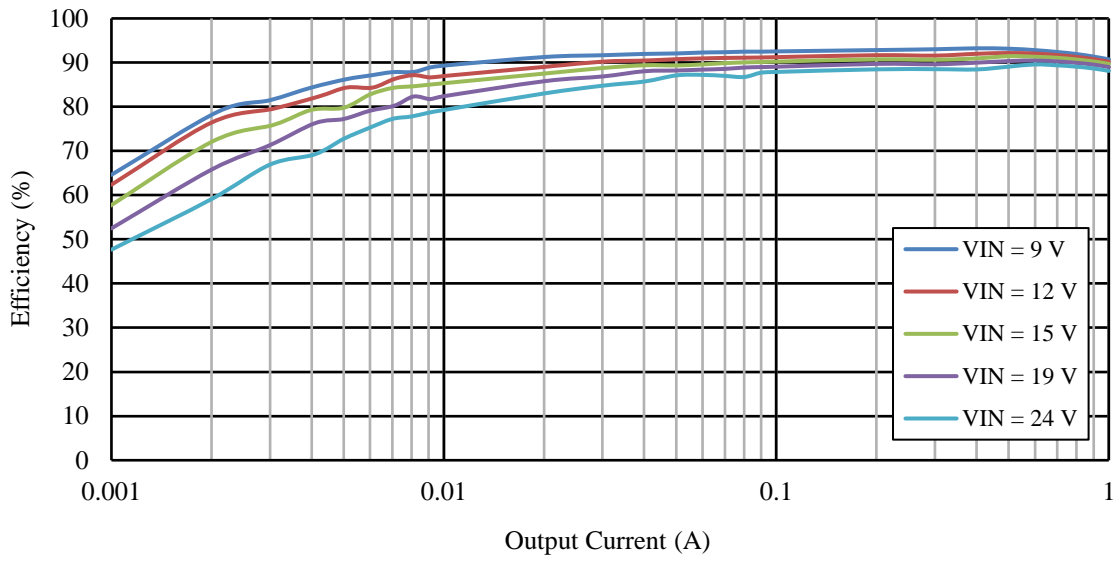


Figure 6-5. Efficiency vs. Output Current

6.5 Load Regulation

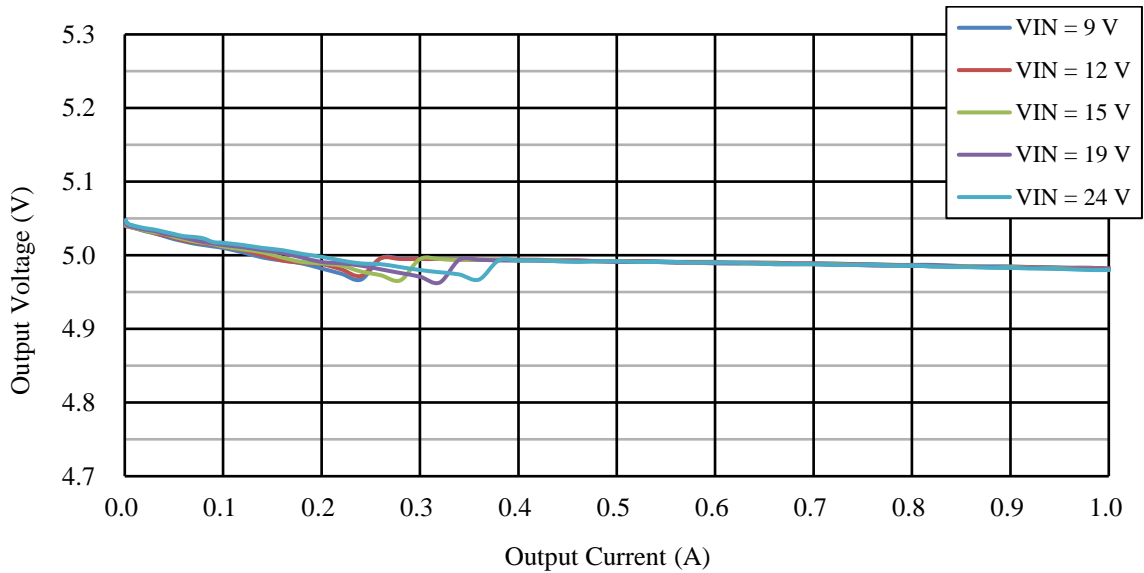


Figure 6-6. Output Voltage vs. Output Current

7. Operation Check

All the performance data contained in this document were measured at a room temperature. Unless specifically noted, $V_{IN} = 12\text{ V}$, $V_{OUT} = 5\text{ V}$.

For more details on the NR263S such as electrical characteristics and operational descriptions, refer to the data sheet.

7.1 Startup Operation

The soft start function is activated at power-on. The soft start period depends on the capacitance of the capacitor connected to the SS pin. Even when the IC starts with the enable function, the soft start function is activated.

Figure 7-1 and Figure 7-2 show the startup waveforms with the UVLO (the EN pin is pulled up to the IN pin) and enable function (external signal is input to the EN pin), respectively.

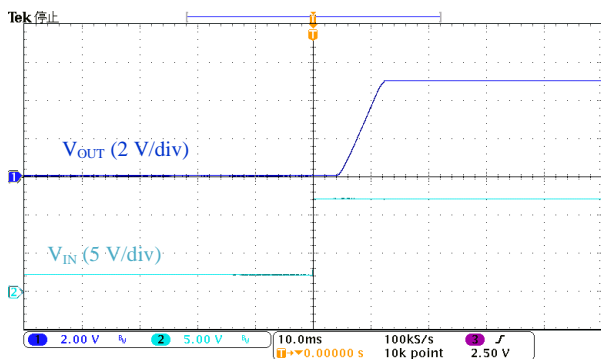


Figure 7-1. Operational Waveforms at Startup by UVLO ($I_{OUT} = 250\text{ mA}$, $C_{SS} = 0.047\text{ }\mu\text{F}$)

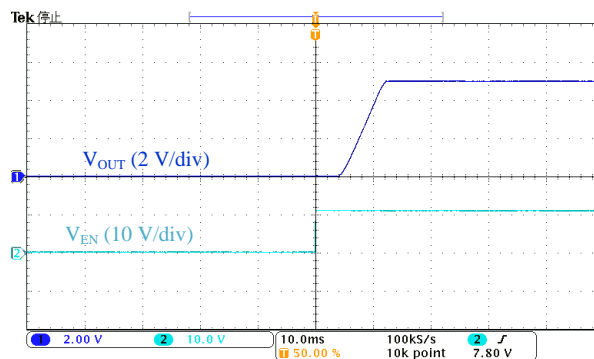


Figure 7-2. Operational Waveforms at Startup by Enable Function ($I_{OUT} = 250\text{ mA}$, $C_{SS} = 0.047\text{ }\mu\text{F}$)

7.2 Switching Operation

Figure 7-7 to Figure 7-3 show the operational waveforms according to the load. The NR263S regulates the output voltage with the current mode PWM control. In a heavy load condition, the IC operates in the continuous conduction mode of PWM frequency of 500 kHz (typ.). In a light load condition, the IC enters the pulse skipping mode that reduces the oscillation frequency to improve efficiency. The minimum on-time is limited to 200 ns (typ.).

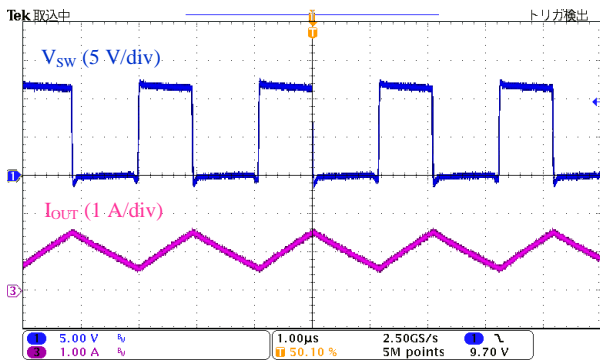


Figure 7-3. Operational Waveforms in Normal Operation ($I_{OUT} = 1$ A)

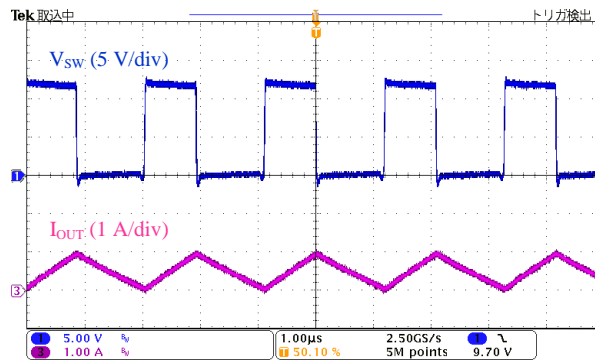


Figure 7-4. Operational Waveforms in Normal Operation ($I_{OUT} = 0.45$ A)

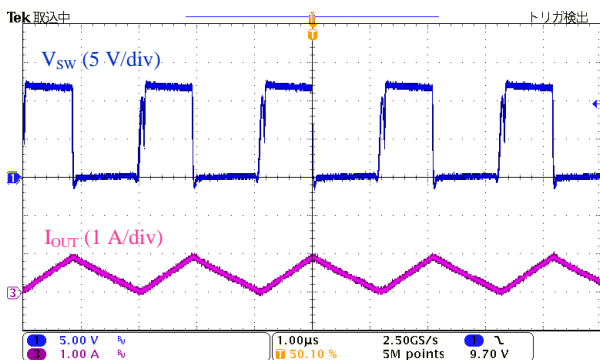


Figure 7-5. Operational Waveforms in Normal Operation ($I_{OUT} = 0.42$ A)

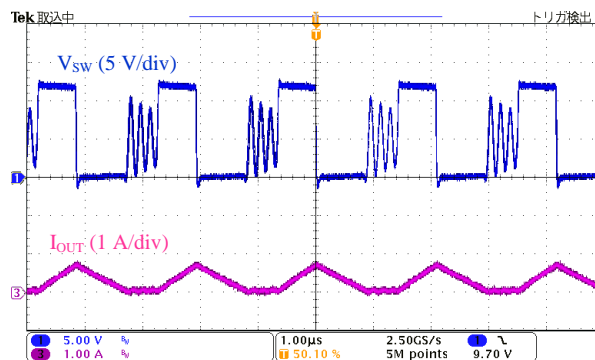


Figure 7-6. Operational Waveforms in Normal Operation ($I_{OUT} = 0.25$ A)

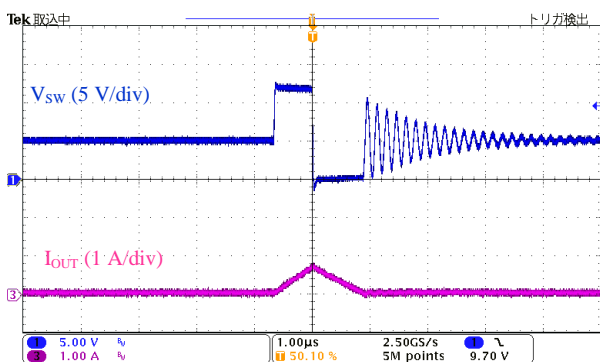


Figure 7-7. Operational Waveforms in Normal Operation ($I_{OUT} = 10$ mA)

7.3 Output Ripple Voltage

The design example has an output ripple voltage of about 20 mV_{P-P}. The bandwidth of the oscilloscope is set to 20 MHz.

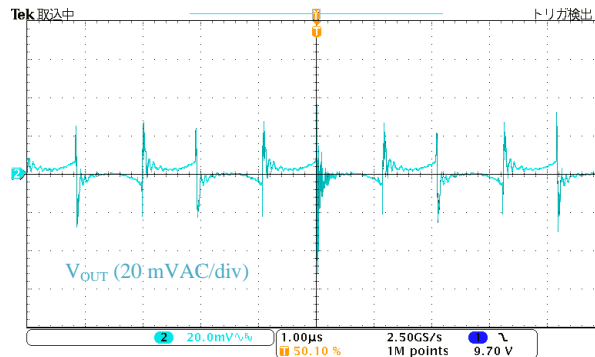


Figure 7-8. Output Ripple Voltage Waveform ($I_{OUT} = 1\text{ A}$)

7.4 Load Transient Reponse

Figure 7-9 to Figure 7-11 show the load transient response waveforms of output voltage when the change rate of the load current is 0.75 A/ms, 7.5 A/ms, and 75 A/ms, respectively.

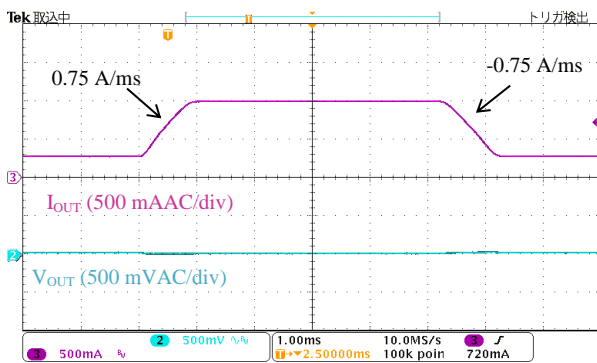


Figure 7-9. Load Transient Response Waveforms (0.75 A/ms)

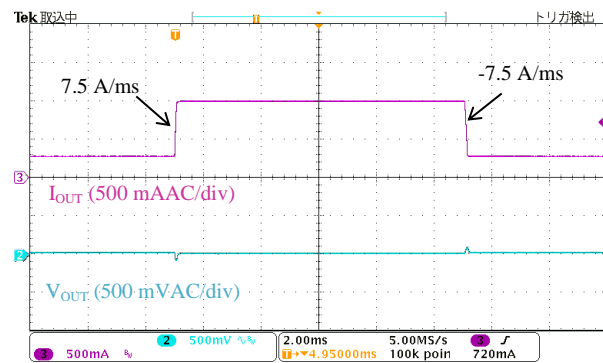


Figure 7-10. Load Transient Response Waveforms (7.5 A/ms)

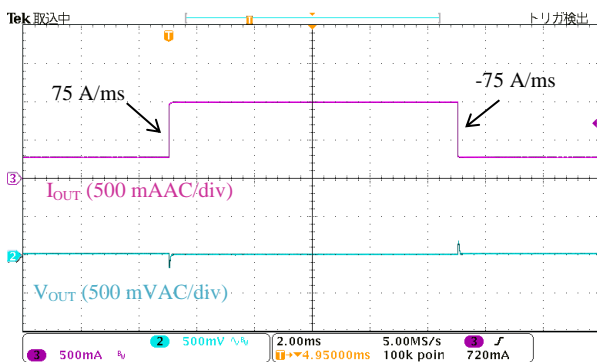


Figure 7-11. Load Transient Response Waveforms (75 A/ms)

Important Notes

- All data, illustrations, graphs, tables and any other information included in this document (the “Information”) as to Sanken’s products listed herein (the “Sanken Products”) are current as of the date this document is issued. The Information is subject to any change without notice due to improvement of the Sanken Products, etc. Please make sure to confirm with a Sanken sales representative that the contents set forth in this document reflect the latest revisions before use.
- The Sanken Products are intended for use as components of general purpose electronic equipment or apparatus (such as home appliances, office equipment, telecommunication equipment, measuring equipment, etc.). Prior to use of the Sanken Products, please put your signature, or affix your name and seal, on the specification documents of the Sanken Products and return them to Sanken. When considering use of the Sanken Products for any applications that require higher reliability (such as transportation equipment and its control systems, traffic signal control systems or equipment, disaster/crime alarm systems, various safety devices, etc.), you must contact a Sanken sales representative to discuss the suitability of such use and put your signature, or affix your name and seal, on the specification documents of the Sanken Products and return them to Sanken, prior to the use of the Sanken Products. The Sanken Products are not intended for use in any applications that require extremely high reliability such as: aerospace equipment; nuclear power control systems; and medical equipment or systems, whose failure or malfunction may result in death or serious injury to people, i.e., medical devices in Class III or a higher class as defined by relevant laws of Japan (collectively, the “Specific Applications”). Sanken assumes no liability or responsibility whatsoever for any and all damages and losses that may be suffered by you, users or any third party, resulting from the use of the Sanken Products in the Specific Applications or in manner not in compliance with the instructions set forth herein.
- In the event of using the Sanken Products by either (i) combining other products or materials or both therewith or (ii) physically, chemically or otherwise processing or treating or both the same, you must duly consider all possible risks that may result from all such uses in advance and proceed therewith at your own responsibility.
- Although Sanken is making efforts to enhance the quality and reliability of its products, it is impossible to completely avoid the occurrence of any failure or defect or both in semiconductor products at a certain rate. You must take, at your own responsibility, preventative measures including using a sufficient safety design and confirming safety of any equipment or systems in/for which the Sanken Products are used, upon due consideration of a failure occurrence rate and derating, etc., in order not to cause any human injury or death, fire accident or social harm which may result from any failure or malfunction of the Sanken Products. Please refer to the relevant specification documents and Sanken’s official website in relation to derating.
- No anti-radioactive ray design has been adopted for the Sanken Products.
- The circuit constant, operation examples, circuit examples, pattern layout examples, design examples, recommended examples, all information and evaluation results based thereon, etc., described in this document are presented for the sole purpose of reference of use of the Sanken Products.
- Sanken assumes no responsibility whatsoever for any and all damages and losses that may be suffered by you, users or any third party, or any possible infringement of any and all property rights including intellectual property rights and any other rights of you, users or any third party, resulting from the Information.
- No information in this document can be transcribed or copied or both without Sanken’s prior written consent.
- Regarding the Information, no license, express, implied or otherwise, is granted hereby under any intellectual property rights and any other rights of Sanken.
- Unless otherwise agreed in writing between Sanken and you, Sanken makes no warranty of any kind, whether express or implied, including, without limitation, any warranty (i) as to the quality or performance of the Sanken Products (such as implied warranty of merchantability, and implied warranty of fitness for a particular purpose or special environment), (ii) that any Sanken Product is delivered free of claims of third parties by way of infringement or the like, (iii) that may arise from course of performance, course of dealing or usage of trade, and (iv) as to the Information (including its accuracy, usefulness, and reliability).
- In the event of using the Sanken Products, you must use the same after carefully examining all applicable environmental laws and regulations that regulate the inclusion or use or both of any particular controlled substances, including, but not limited to, the EU RoHS Directive, so as to be in strict compliance with such applicable laws and regulations.
- You must not use the Sanken Products or the Information for the purpose of any military applications or use, including but not limited to the development of weapons of mass destruction. In the event of exporting the Sanken Products or the Information, or providing them for non-residents, you must comply with all applicable export control laws and regulations in each country including the U.S. Export Administration Regulations (EAR) and the Foreign Exchange and Foreign Trade Act of Japan, and follow the procedures required by such applicable laws and regulations.
- Sanken assumes no responsibility for any troubles, which may occur during the transportation of the Sanken Products including the falling thereof, out of Sanken’s distribution network.
- Although Sanken has prepared this document with its due care to pursue the accuracy thereof, Sanken does not warrant that it is error free and Sanken assumes no liability whatsoever for any and all damages and losses which may be suffered by you resulting from any possible errors or omissions in connection with the Information.
- Please refer to our official website in relation to general instructions and directions for using the Sanken Products, and refer to the relevant specification documents in relation to particular precautions when using the Sanken Products.
- All rights and title in and to any specific trademark or tradename belong to Sanken and such original right holder(s).

DSGN-CEZ-16003